

## MCP16311/2 Inverting Buck-Boost Application

Author: Andreea Macalau  
Microchip Technology Inc.

### INTRODUCTION

This document describes the implementation of an inverting buck-boost topology, using the MCP16311/2 synchronous buck switching regulator. Generally, a buck converter is used to derive the required supply voltage level from a higher input voltage. However, there are several applications where a negative input supply is necessary; in this case, a topology such as an inverting buck-boost converter can be implemented, for which the output voltage is negative with respect to the ground.

The proposed application circuit can be used to supply a negative output voltage for devices such as: line drivers and receivers, instrumentation amplifiers, audio amplifiers, etc.

### BASIC BUCK CONFIGURATION

To understand the functionality of an inverting buck-boost topology, a short explanation of the buck topology is necessary.

In [Figure 1](#), when the high-side switch ( $S_1$ ) is turned on and the low-side switch ( $S_2$ ) is turned off (red loop), a DC voltage ( $V_{IN} - V_{OUT}$ ) is applied to the inductor ( $L$ ), resulting in a positive linear ramp of inductor current, given by [Equation 1](#).

#### EQUATION 1: INDUCTOR CURRENT VARIATION DURING ON TIME

$$\frac{di}{dt} = \frac{V_{IN} - V_{OUT}}{L}$$

When the high-side switch ( $S_1$ ) turns off and the low-side switch ( $S_2$ ) turns on (blue loop), the applied inductor voltage is equal to  $-V_{OUT}$ , resulting in a negative linear ramp of inductor current, as shown in [Equation 2](#).

#### EQUATION 2: INDUCTOR CURRENT VARIATION DURING OFF TIME

$$\frac{di}{dt} = -\frac{V_{OUT}}{L}$$


[Equation 3](#) represents the peak-to-peak current flowing through the inductor.

#### EQUATION 3: PEAK-TO-PEAK INDUCTOR CURRENT

$$I_{L(PP)} = \frac{(V_{IN} - V_{OUT}) \times D}{f_{SW} \times L}$$

Where:

- D = Duty cycle
- $f_{SW}$  = Switching frequency
- $V_{IN}$  = Input voltage
- $V_{OUT}$  = Output voltage
- L = Inductance

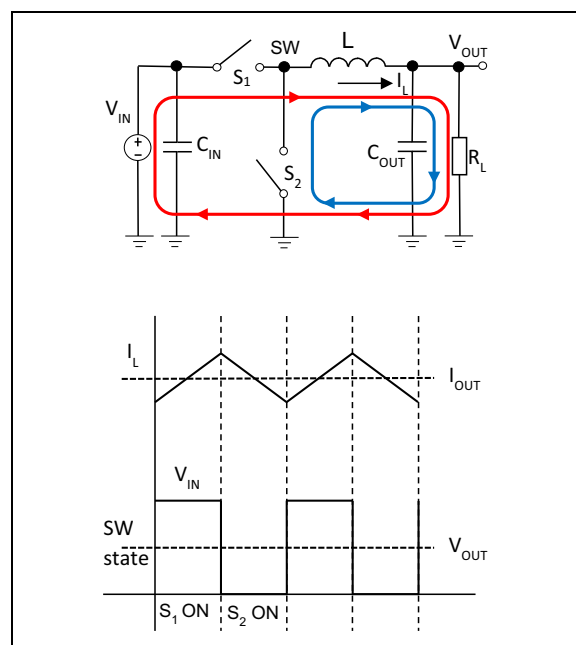

**FIGURE 1:** Buck Circuit and Waveforms In Continuous Conduction Mode (CCM).

## INVERTING BUCK-BOOST CONFIGURATION

A possible implementation of an inverting buck-boost converter, which is derived from a buck regulator, can be seen in [Figure 2](#) and its functionality is described in the following paragraphs.

When the high-side switch ( $S_1$ ) is turned on and the low-side switch ( $S_2$ ) is turned off (red loop), the voltage applied across the inductor is  $V_{IN}$ , resulting in a positive linear ramp of inductor current, given by [Equation 4](#).

### EQUATION 4: INDUCTOR CURRENT VARIATION DURING ON TIME

$$\frac{di}{dt} = \frac{V_{IN}}{L}$$

When the high-side switch ( $S_1$ ) turns off and the low-side switch ( $S_2$ ) turns on (blue loop), the applied inductor voltage is equal to  $-V_{OUT}$ , resulting in a negative linear ramp of inductor current, as shown in [Equation 5](#).

### EQUATION 5: INDUCTOR CURRENT VARIATION DURING OFF TIME

$$\frac{di}{dt} = -\frac{V_{OUT}}{L}$$

The peak-to-peak current flowing through the inductor is given by [Equation 6](#).

### EQUATION 6: PEAK-TO-PEAK INDUCTOR CURRENT

$$I_{L(PP)} = \frac{V_{IN} \times D}{f_{SW} \times L}$$

[Equation 7](#) represents the approximation of the duty cycle for the inverting Buck-Boost converter.

### EQUATION 7: DUTY CYCLE


$$D = \frac{|V_{OUT}|}{V_{IN} + |V_{OUT}|}$$

## DESIGN CONSIDERATIONS

### Input Voltage Range

For implementing a buck-boost topology using a buck switching regulator, the GND pin of the converter will be tied to  $V_{OUT}$  and the positive lead of the output capacitor will be connected to GND.

In this case, the voltage applied on the supply pin of the converter will be  $V_{IN} - (-V_{OUT})$  and not  $V_{IN}$ , as for a typical buck application. This means that the maximum input voltage for an inverting buck-boost converter is limited to  $V_{IN} - |V_{OUT}|$ .

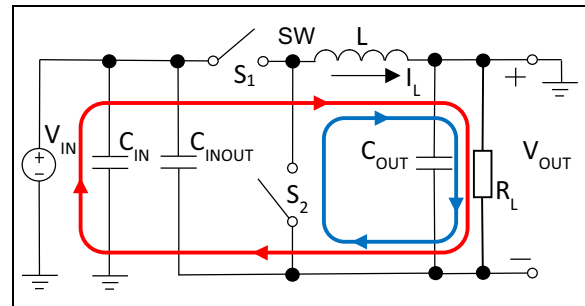

**FIGURE 2:** The Proposed Inverting Buck-Boost Circuit.

Considering that the output voltage is negative, the operating duty cycle can be defined by using [Equation 8](#).

### EQUATION 8: DUTY CYCLE FOR AN INVERTING BUCK-BOOST

$$D = \frac{V_{OUT}}{V_{OUT} - V_{IN}}$$

For a buck converter, the average inductor current is equal to the load current ( $I_{LOAD}$ ). By contrast, in the case of an inverting buck-boost converter, the average inductor current is equal to  $I_{LOAD}/(1 - D)$ .

## Right Half Plane Zero (RHPZ) Effect

An important factor that must be considered is the behavior of this proposed circuit when operating in continuous and discontinuous conduction mode (DCM). Designs that are stable in the discontinuous mode may become unstable when the load increases and the transition to the continuous mode is done.

When the buck converter is used in a buck-boost design, a Right Half Plane Zero (RHPZ) is introduced. In this case, the gain of the loop is not affected. However, it causes a phase drop which will affect the stability of the system.

### RHPZ in DCM

While operating in DCM, the frequency of the RHPZ is high enough so as to not affect the functionality.

During the on time, the inductor is charging, while the output capacitor is discharging. If there is any sudden change (an increase) of the duty cycle, the inductor current will go to a higher value, which will generate a higher drop on  $V_{OUT}$  (see Figure 3). However, because the level of the inductor current is higher, the increasing slope of  $V_{OUT}$  is steeper and the output voltage will achieve the required value during the off time. By operating in DCM, the drop on  $V_{OUT}$  caused by the RHPZ is not visible.

### RHPZ in CCM

When running in CCM, if there is a sudden increase of the on time (because the off time is shorter), a drop on  $V_{OUT}$  can be noticed. Even though the slope of  $V_{OUT}$  is steeper (because of the higher level of the inductor current), the output voltage at that moment in time is still too low compared to the value before, as shown in Figure 3.

Whenever the on time is increased, the output voltage will drop initially and during the next cycles it will achieve the corresponding level; this is not acceptable for a feedback-controlled system, because during this drop, the loop will encounter a positive feedback and the system will tend to oscillate.

To eliminate the effects of the RHPZ for this kind of applications (an inverting buck-boost design), a bypass capacitor must be connected between  $V_{IN}$  and  $V_{OUT}$ .

The value of this capacitor must be significantly lower than the input capacitor ( $C_{IN}$ ) and its voltage rating must be greater than  $V_{IN} + |V_{OUT}|$ .


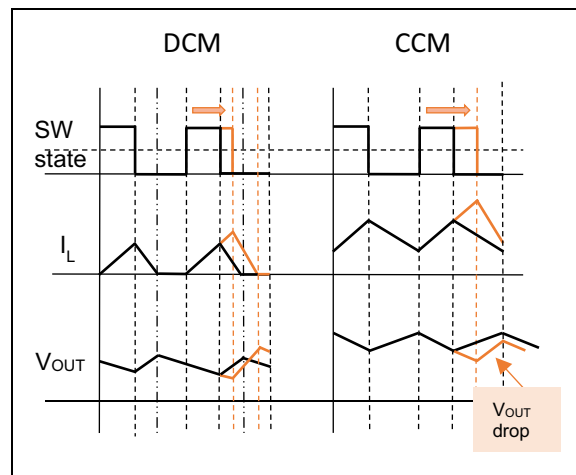


FIGURE 3: RHPZ in DCM vs. CCM.


## APPLICATION INFORMATION

The circuit diagram of the proposed application is detailed in [Figure 4](#).

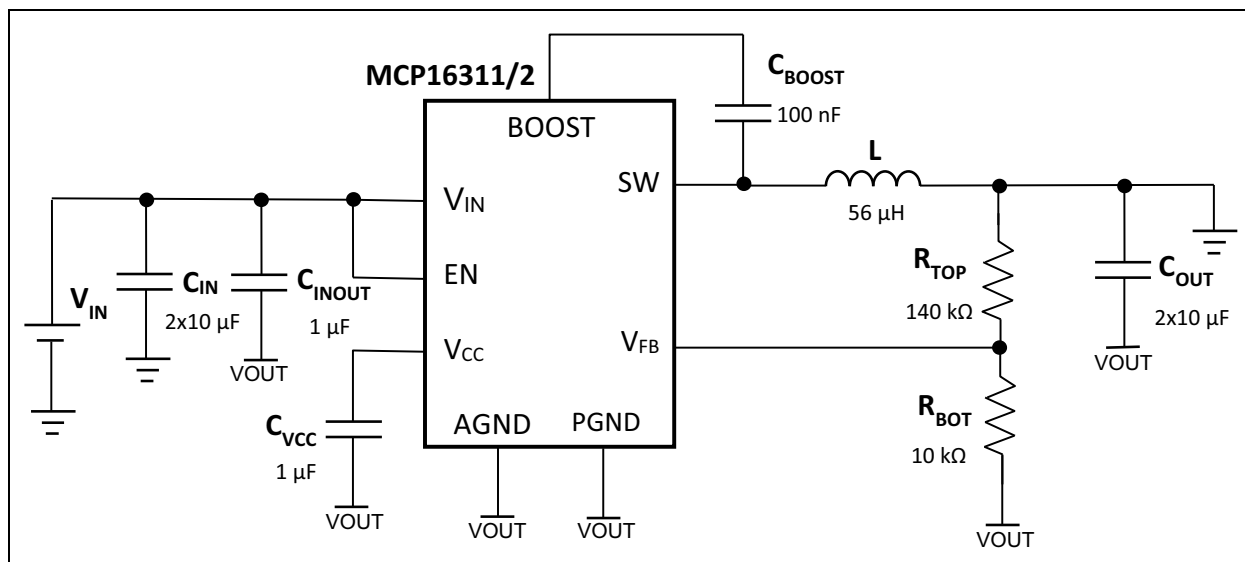

**FIGURE 4:** MCP16311/2 Inverting Buck-Boost Application Circuit Diagram.

The physical implementation of the converter on a board, for this design, is shown in [Figure 5](#).

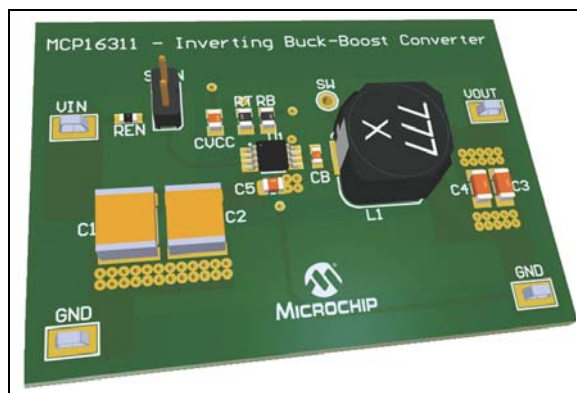


**FIGURE 5:** MCP16311 Inverting Buck-Boost Converter Board.

## APPLICATION EXAMPLE


- Input voltage range: 4.4V – 18V
- Output voltage: –12V
- Output current:
  - 0.32A @  $V_{IN} = 8V$ ,  $T_{AMB} = +25^{\circ}C$
  - 0.5A @  $V_{IN} = 12V$ ,  $T_{AMB} = +25^{\circ}C$
  - 0.54A @  $V_{IN} = 16V$ ,  $T_{AMB} = +25^{\circ}C$

The Maximum Output Current vs. Input Voltage curve (at 25°C) is presented in [Figure 6](#).

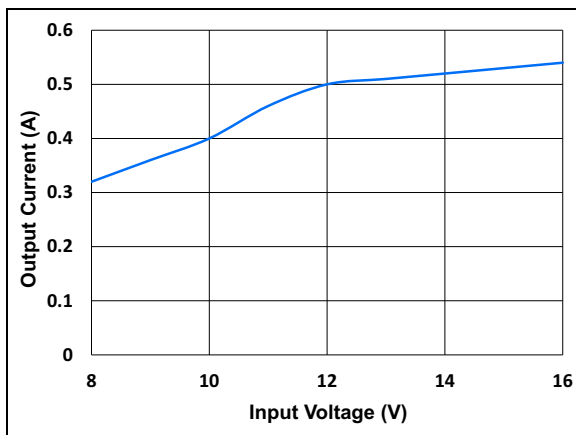

**FIGURE 6:** Maximum Output Current vs. Input Voltage @  $T_{AMB} = +25^{\circ}C$ .

The Efficiency vs. Output Current graph, measured at an ambient temperature of 25°C, is shown in [Figure 7](#).

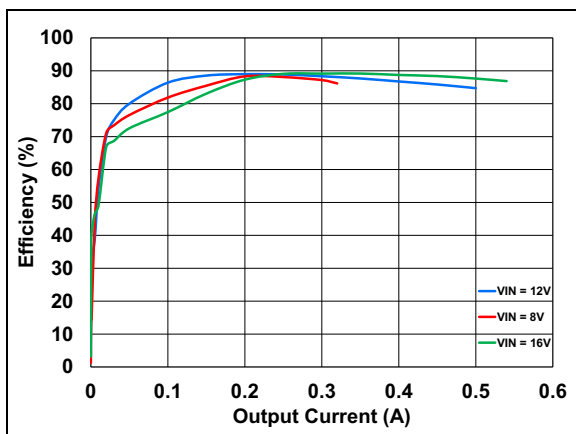

**FIGURE 7:** Efficiency vs. Output Current @  $T_{AMB} = +25^{\circ}C$ .

## CONCLUSIONS

This technical brief presents the utilization of an MCP16311/2 synchronous buck switching regulator in an inverting buck-boost design implementation. The proposed circuit reflects the main advantages of this type of application: buck and boost capabilities, negative output voltage with respect to the input, while utilizing only one additional passive component. By contrast to a regular buck typology, such an implementation offers lower current capabilities and a lower input voltage range. However, the MCP16311/2 synchronous buck switching regulator can be a viable solution for an inverting buck-boost application thanks to its high versatility, with minimum additional components needed.

## REFERENCES

- MCP16311/2 Data Sheet – “30V Input, 1A Output, High-Efficiency, Integrated Synchronous Switch Step-Down Regulator” (DS20005255)
- AN2102 – “Designing Applications with MCP16331 High-Input Voltage Buck Converter” (DS00002102)

NOTES:

---

**Note the following details of the code protection feature on Microchip devices:**

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is secure when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods being used in attempts to breach the code protection features of the Microchip devices. We believe that these methods require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Attempts to breach these code protection features, most likely, cannot be accomplished without violating Microchip's intellectual property rights.
- Microchip is willing to work with any customer who is concerned about the integrity of its code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is "unbreakable." Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

Information contained in this publication is provided for the sole purpose of designing with and using Microchip products. Information regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications.

THIS INFORMATION IS PROVIDED BY MICROCHIP "AS IS". MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDIRECT, SPECIAL, PUNITIVE, INCIDENTAL OR CONSEQUENTIAL LOSS, DAMAGE, COST OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP'S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

**Trademarks**

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, chipKIT, chipKIT logo, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Kleer, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PackTime, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AgileSwitch, APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, FlashTec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, Augmented Switching, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, Espresso T1S, EtherGREEN, IdealBridge, In-Circuit Serial Programming, ICSP, INICnet, Intelligent Paralleling, Inter-Chip Connectivity, JitterBlocker, maxCrypto, maxView, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, RTAX, RTG4, SAM-ICE, Serial Quad I/O, simpleMAP, SimpliPHY, SmartBuffer, SMART-I.S., storClad, SQI, SuperSwitcher, SuperSwitcher II, Switchtec, SynchroPHY, Total Endurance, TSHARC, USBCheck, VariSense, VectorBlox, VeriPHY, ViewSpan, WiperLock, XpressConnect, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2021, Microchip Technology Incorporated, All Rights Reserved.

ISBN: 978-1-5224-7521-7

For information regarding Microchip's Quality Management Systems, please visit [www.microchip.com/quality](http://www.microchip.com/quality).

## Worldwide Sales and Service

### AMERICAS

**Corporate Office**  
2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200  
Fax: 480-792-7277  
Technical Support:  
<http://www.microchip.com/support>  
Web Address:  
[www.microchip.com](http://www.microchip.com)

**Atlanta**  
Duluth, GA  
Tel: 678-957-9614  
Fax: 678-957-1455

**Austin, TX**  
Tel: 512-257-3370

**Boston**  
Westborough, MA  
Tel: 774-760-0087  
Fax: 774-760-0088

**Chicago**  
Itasca, IL  
Tel: 630-285-0071  
Fax: 630-285-0075

**Dallas**  
Addison, TX  
Tel: 972-818-7423  
Fax: 972-818-2924

**Detroit**  
Novi, MI  
Tel: 248-848-4000

**Houston, TX**  
Tel: 281-894-5983

**Indianapolis**  
Noblesville, IN  
Tel: 317-773-8323  
Fax: 317-773-5453  
Tel: 317-536-2380

**Los Angeles**  
Mission Viejo, CA  
Tel: 949-462-9523  
Fax: 949-462-9608  
Tel: 951-273-7800

**Raleigh, NC**  
Tel: 919-844-7510

**New York, NY**  
Tel: 631-435-6000

**San Jose, CA**  
Tel: 408-735-9110  
Tel: 408-436-4270

**Canada - Toronto**  
Tel: 905-695-1980  
Fax: 905-695-2078

### ASIA/PACIFIC

**Australia - Sydney**  
Tel: 61-2-9868-6733

**China - Beijing**  
Tel: 86-10-8569-7000

**China - Chengdu**  
Tel: 86-28-8665-5511

**China - Chongqing**  
Tel: 86-23-8980-9588

**China - Dongguan**  
Tel: 86-769-8702-9880

**China - Guangzhou**  
Tel: 86-20-8755-8029

**China - Hangzhou**  
Tel: 86-571-8792-8115

**China - Hong Kong SAR**  
Tel: 852-2943-5100

**China - Nanjing**  
Tel: 86-25-8473-2460

**China - Qingdao**  
Tel: 86-532-8502-7355

**China - Shanghai**  
Tel: 86-21-3326-8000

**China - Shenyang**  
Tel: 86-24-2334-2829

**China - Shenzhen**  
Tel: 86-755-8864-2200

**China - Suzhou**  
Tel: 86-186-6233-1526

**China - Wuhan**  
Tel: 86-27-5980-5300

**China - Xian**  
Tel: 86-29-8833-7252

**China - Xiamen**  
Tel: 86-592-2388138

**China - Zhuhai**  
Tel: 86-756-3210040

### ASIA/PACIFIC

**India - Bangalore**  
Tel: 91-80-3090-4444

**India - New Delhi**  
Tel: 91-11-4160-8631

**India - Pune**  
Tel: 91-20-4121-0141

**Japan - Osaka**  
Tel: 81-6-6152-7160

**Japan - Tokyo**  
Tel: 81-3-6880-3770

**Korea - Daegu**  
Tel: 82-53-744-4301

**Korea - Seoul**  
Tel: 82-2-554-7200

**Malaysia - Kuala Lumpur**  
Tel: 60-3-7651-7906

**Malaysia - Penang**  
Tel: 60-4-227-8870

**Philippines - Manila**  
Tel: 63-2-634-9065

**Singapore**  
Tel: 65-6334-8870

**Taiwan - Hsin Chu**  
Tel: 886-3-577-8366

**Taiwan - Kaohsiung**  
Tel: 886-7-213-7830

**Taiwan - Taipei**  
Tel: 886-2-2508-8600

**Thailand - Bangkok**  
Tel: 66-2-694-1351

**Vietnam - Ho Chi Minh**  
Tel: 84-28-5448-2100

### EUROPE

**Austria - Wels**  
Tel: 43-7242-2244-39  
Fax: 43-7242-2244-393

**Denmark - Copenhagen**  
Tel: 45-4485-5910  
Fax: 45-4485-2829

**Finland - Espoo**  
Tel: 358-9-4520-820

**France - Paris**  
Tel: 33-1-69-53-63-20  
Fax: 33-1-69-30-90-79

**Germany - Garching**  
Tel: 49-8931-9700

**Germany - Haan**  
Tel: 49-2129-3766400

**Germany - Heilbronn**  
Tel: 49-7131-72400

**Germany - Karlsruhe**  
Tel: 49-721-625370

**Germany - Munich**  
Tel: 49-89-627-144-0  
Fax: 49-89-627-144-44

**Germany - Rosenheim**  
Tel: 49-8031-354-560

**Israel - Ra'anana**  
Tel: 972-9-744-7705

**Italy - Milan**  
Tel: 39-0331-742611  
Fax: 39-0331-466781

**Italy - Padova**  
Tel: 39-049-7625286

**Netherlands - Drunen**  
Tel: 31-416-690399  
Fax: 31-416-690340

**Norway - Trondheim**  
Tel: 47-7288-4388

**Poland - Warsaw**  
Tel: 48-22-3325737

**Romania - Bucharest**  
Tel: 40-21-407-87-50

**Spain - Madrid**  
Tel: 34-91-708-08-90  
Fax: 34-91-708-08-91

**Sweden - Gothenberg**  
Tel: 46-31-704-60-40

**Sweden - Stockholm**  
Tel: 46-8-5090-4654

**UK - Wokingham**  
Tel: 44-118-921-5800  
Fax: 44-118-921-5820